


Date:

**EXPERIMENT NO .3****AIM:** Implement Arithmetic and Logic unit in Logisim.**Application Example:** Design a calculator that can add, subtract, and perform basic logic operations on two 4-bit numbers.**TABLES OF CALCULATIONS:****1.Arithmetic Circuit**


S1	S0	Cin	Y	Output	Microoperation

**2. Logical Circuit**

<b>S1</b>	<b>S0</b>	<b>Output</b>	<b>Operations</b>

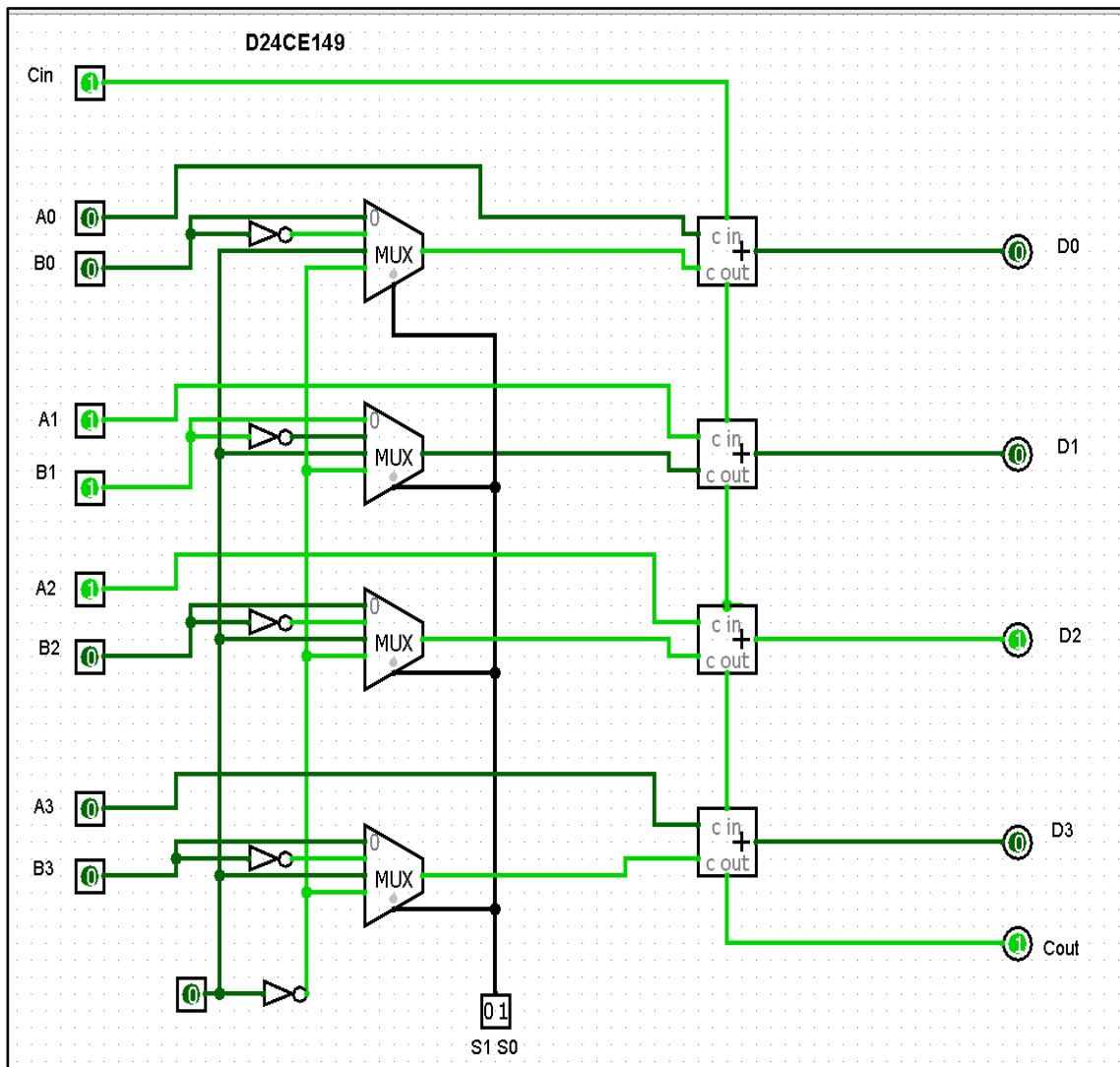
**CIRCUITS:****1.Arithmetic Circuit:**


## 2. Logical Circuit:

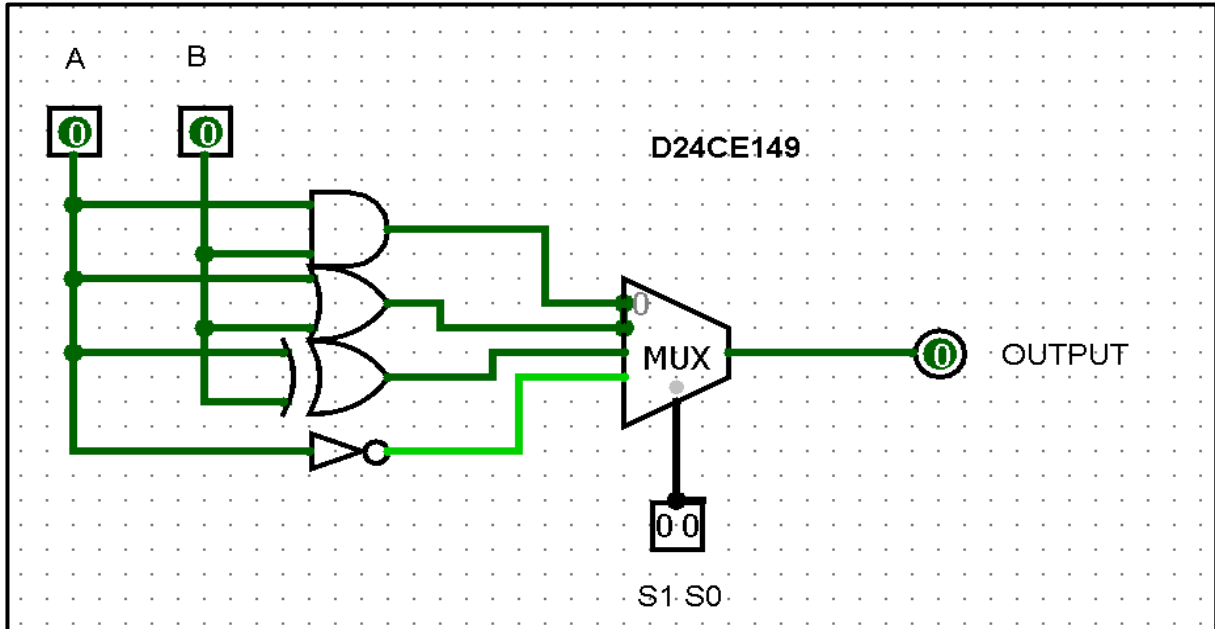

## OUTPUTS:

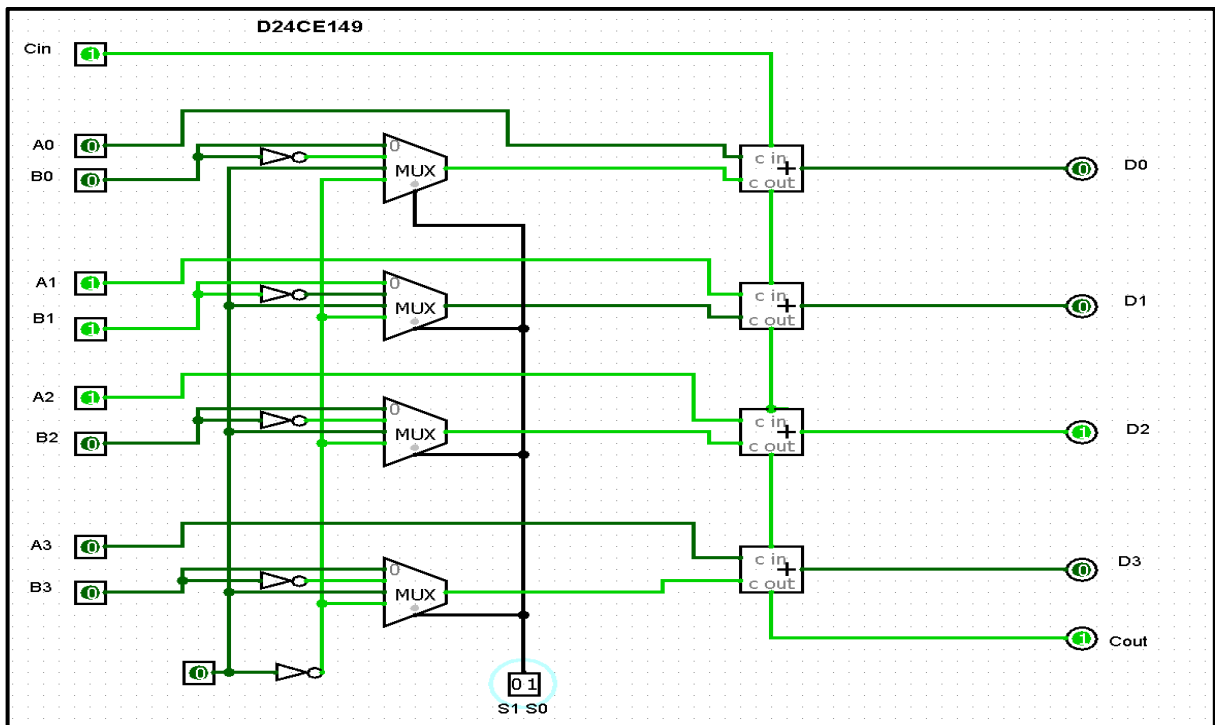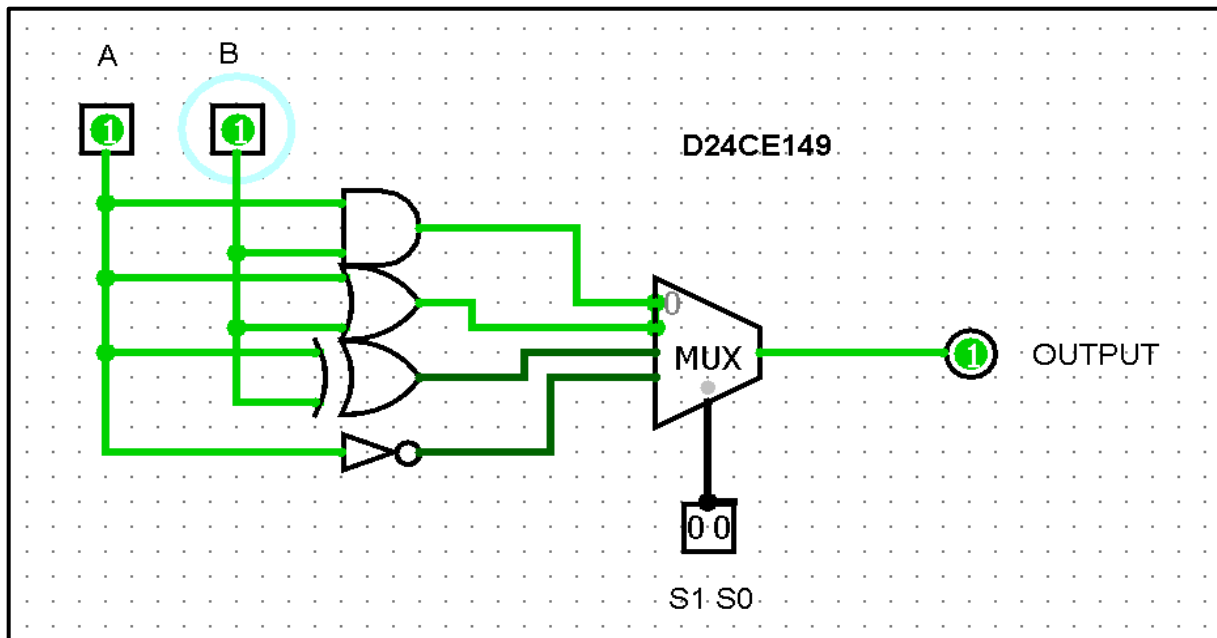Task 1:  $A=6(0110)-B=4(0010)=D=4(0100)$ ;

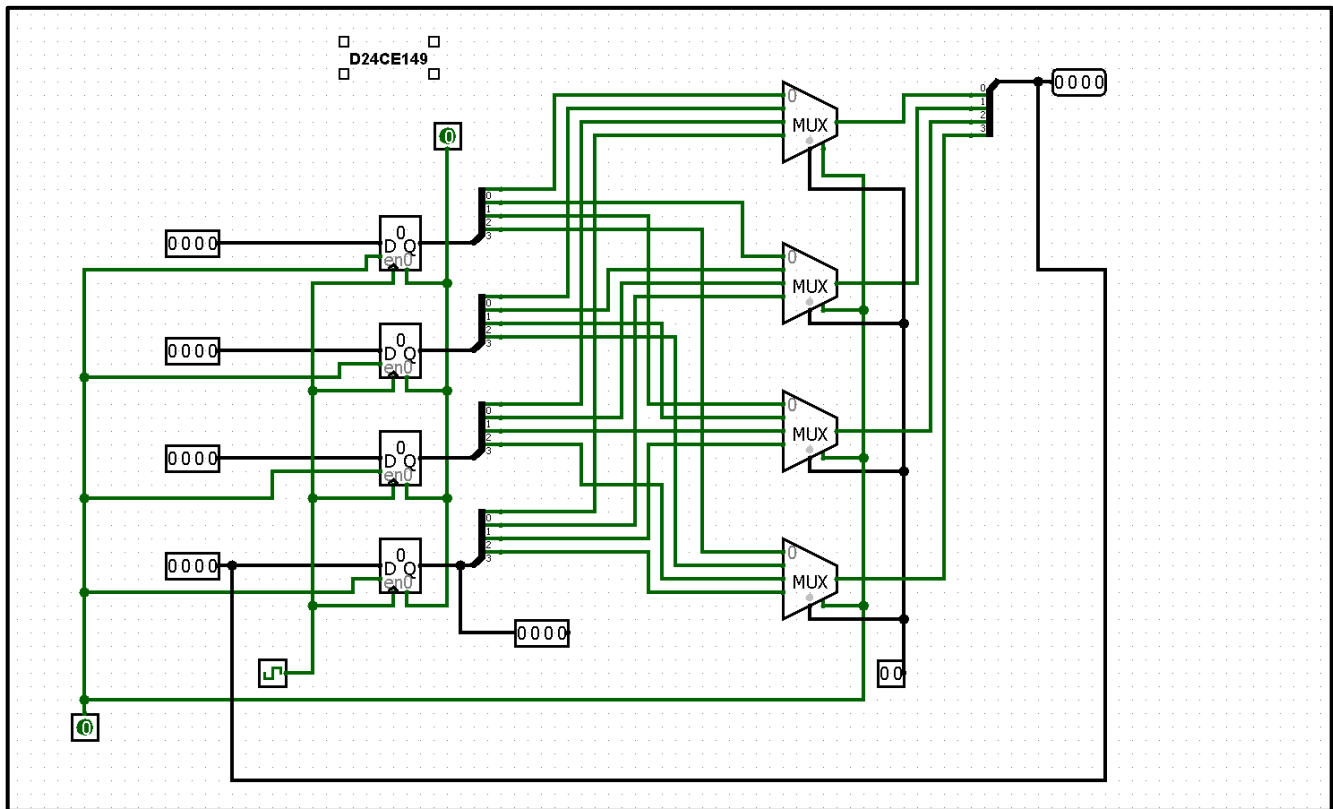



**Task 2: A and B ;****OBSERVATION:****CONCLUSION:**


Date:

**EXPERIMENT NO .4**

AIM: Implement common bus system using Multiplexer in Logisim.

**CIRCUITS:**

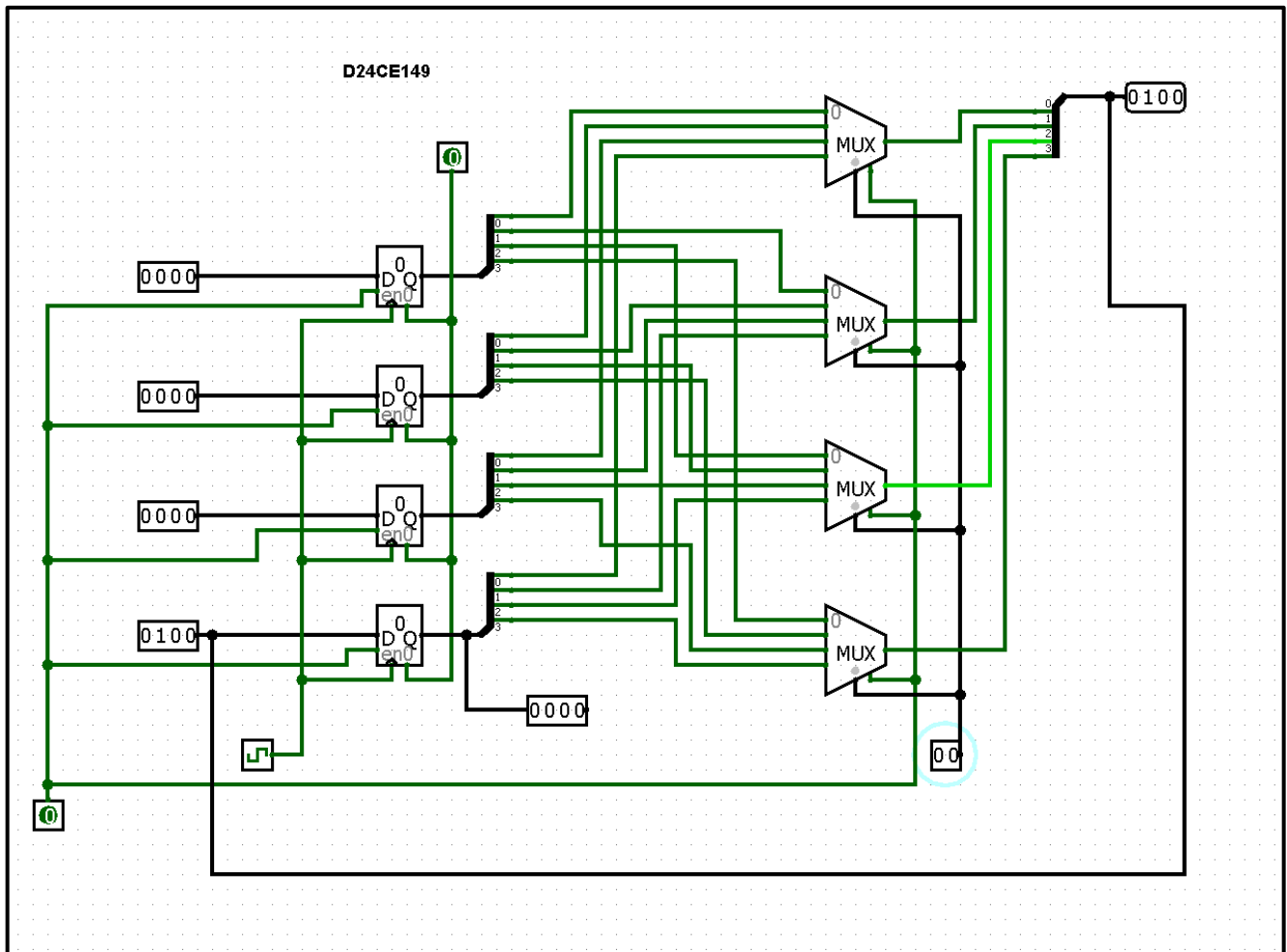**OUTPUTS:**

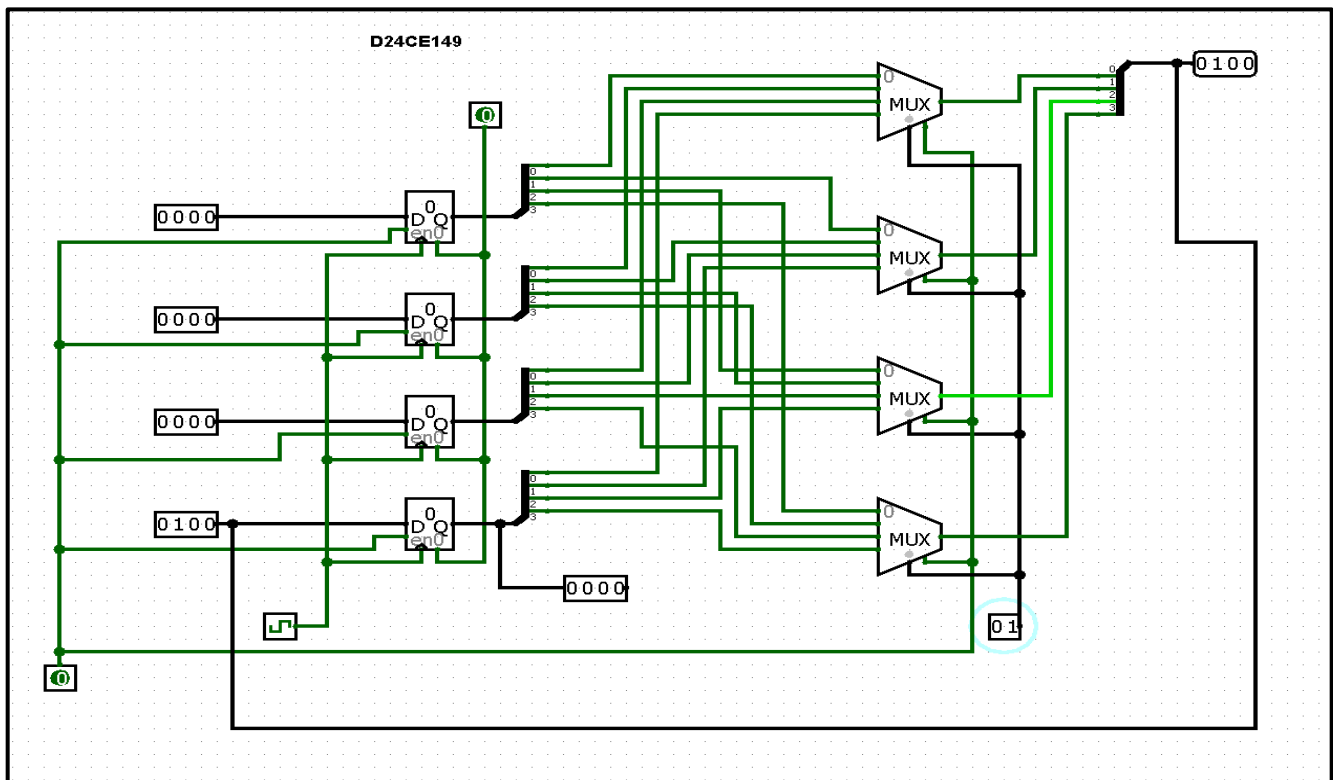

**OBSERVATION**

**CONCLUSION**